


Tessa Vincent
EEET.222: Lab 3
Professor Cliver
Due Date: 3/30/2021

Cutoff Frequency Week 1:

RC High-pass Filter Design Tool - Result -

Calculated the Transfer Function for the RC High-pass filter, displayed on graphs, showing Bode diagram, Nyquist diagram, Impulse response and Step response

CR Filter

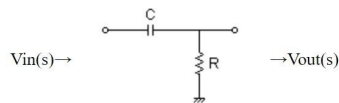

Transfer Function:

$$G(s) = \frac{s}{s+40}$$

Cut-off frequency

$$f_c = 6.3661977236758[\text{Hz}]$$

Rise/Fall time of step response

R = Ω C = F
Stead-state value: % \rightarrow %

Calculate


$$tr = \text{0.057564627324851} [\text{sec}]$$

Cutoff Frequency Week 2:

RC High-pass Filter Design Tool - Result -

Calculated the Transfer Function for the RC High-pass filter, displayed on graphs, showing Bode diagram, Nyquist diagram, Impulse response and Step response

CR Filter

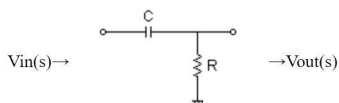

Transfer Function:

$$G(s) = \frac{s}{s+21.276595744681}$$

Cut-off frequency

$$f_c = 3.3862753849339[\text{Hz}]$$

Rise/Fall time of step response


R = Ω C = F
Stead-state value: % \rightarrow %

Calculate

$$tr = \text{0.10822149937072} [\text{sec}]$$

Single Frequency Sound

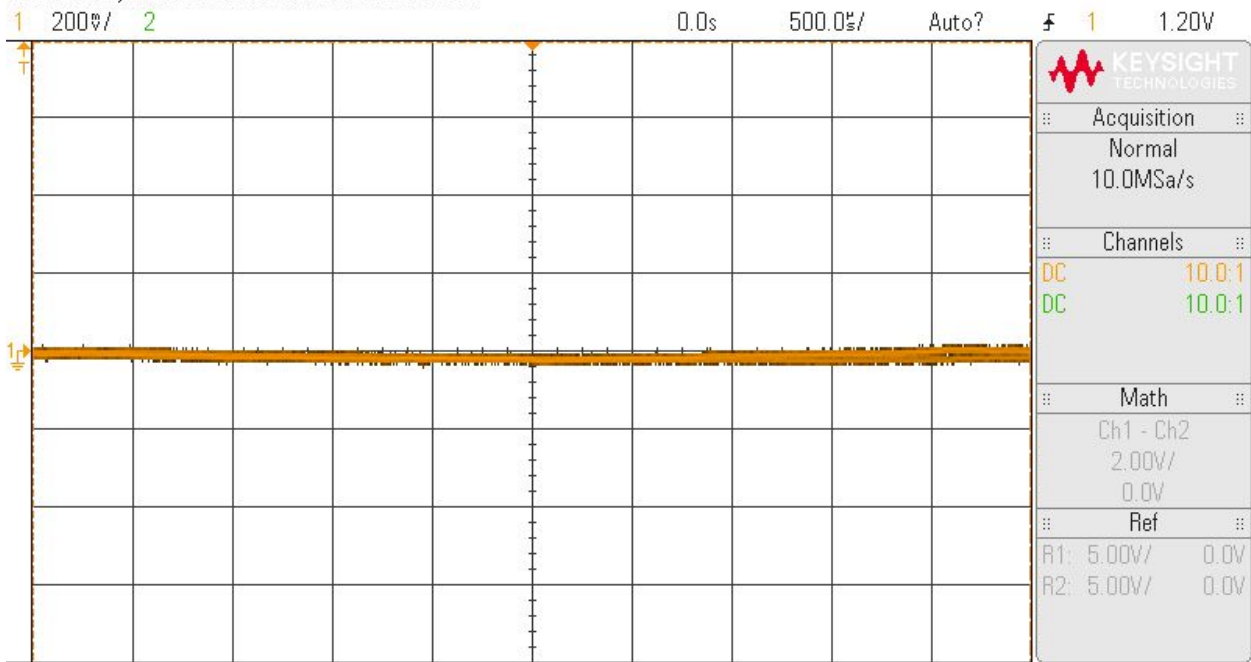
EDU-X 1002A, CN57350228: Wed Mar 24 06:29:16 2021



Freq(1): Low signal

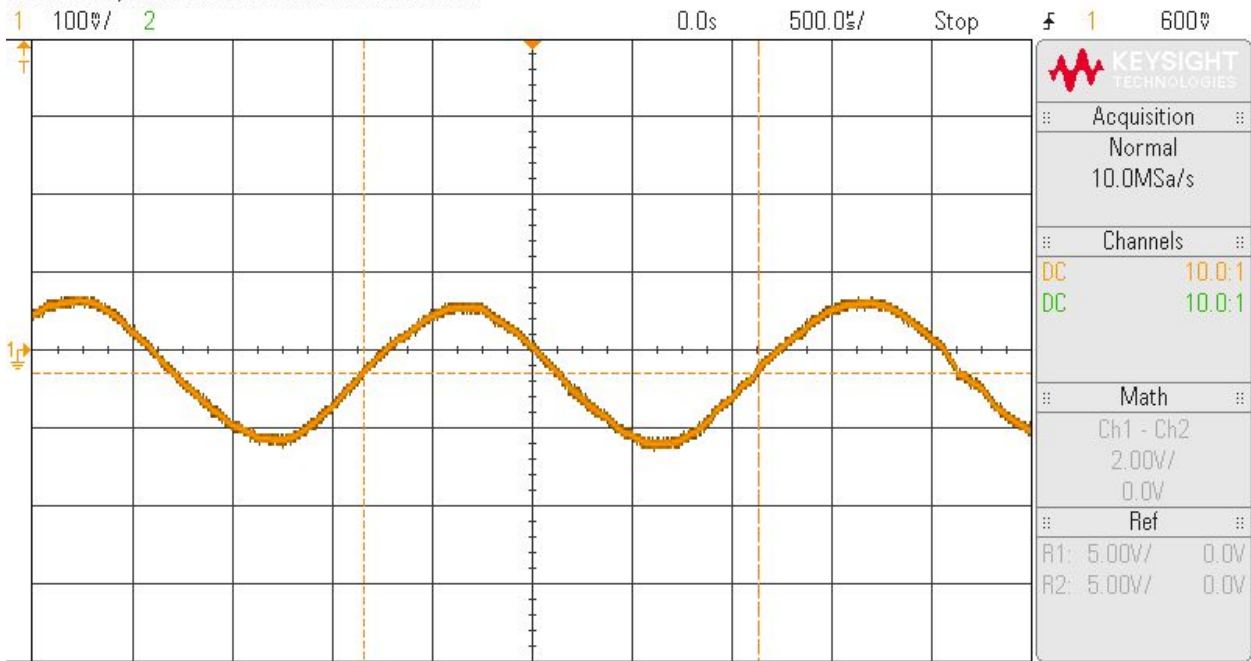06:29 AM
Mar 24, 2021



EDU-X 1002A, CN57350228: Wed Mar 24 06:29:59 2021



Freq(1): 506.66Hz


06:29 AM
Mar 24, 2021

Single Frequency Sound - Shifted by 2.5V

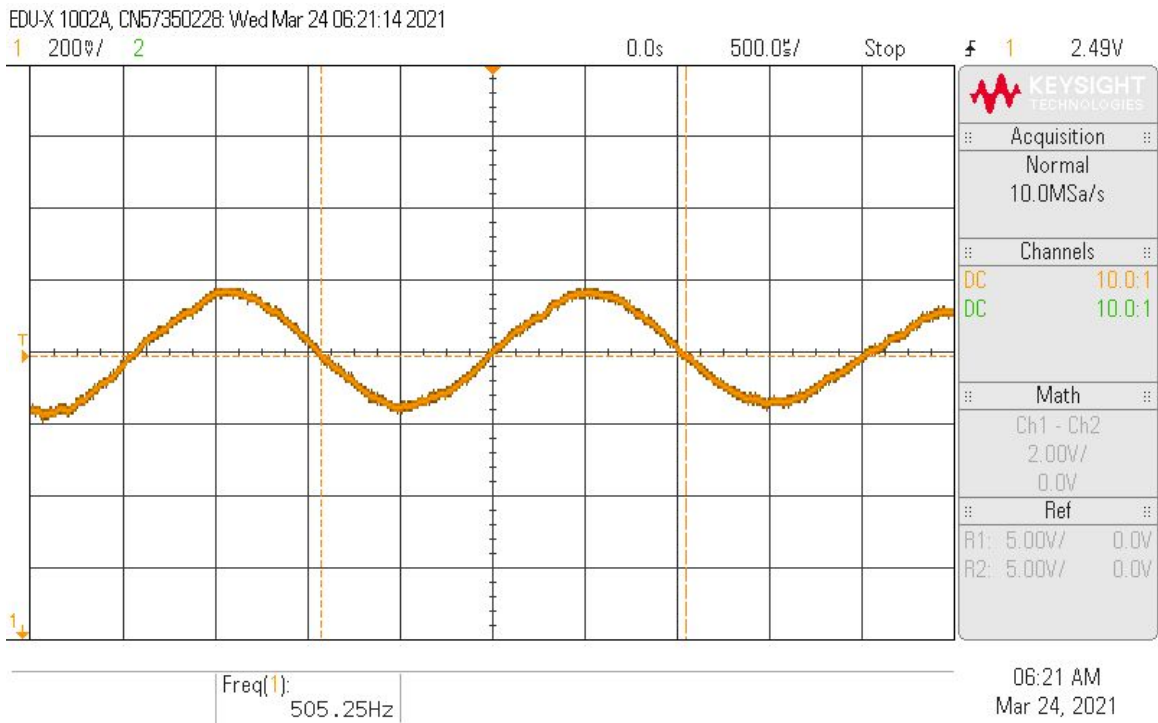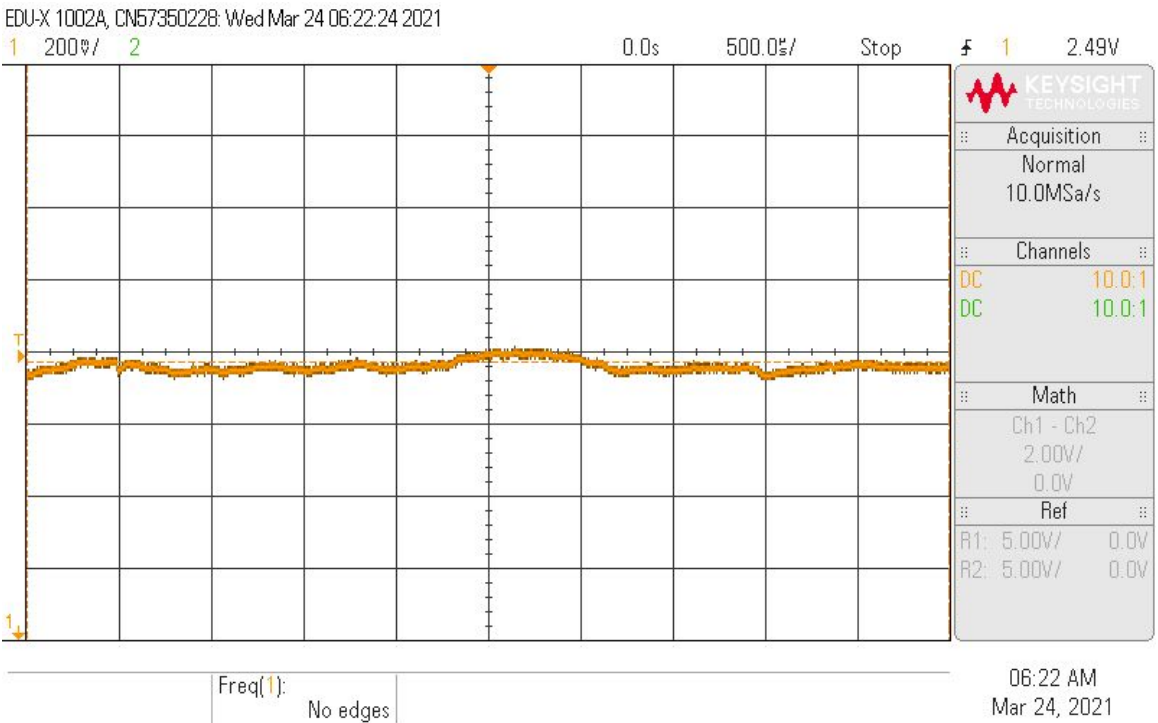


High Pass Filter:


1Hz

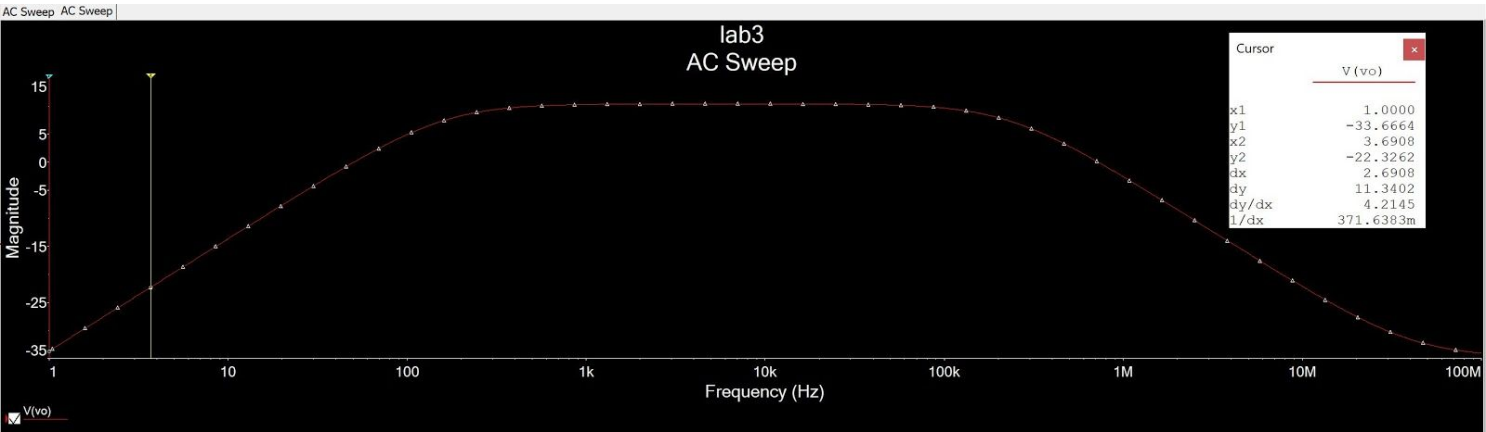


10Hz

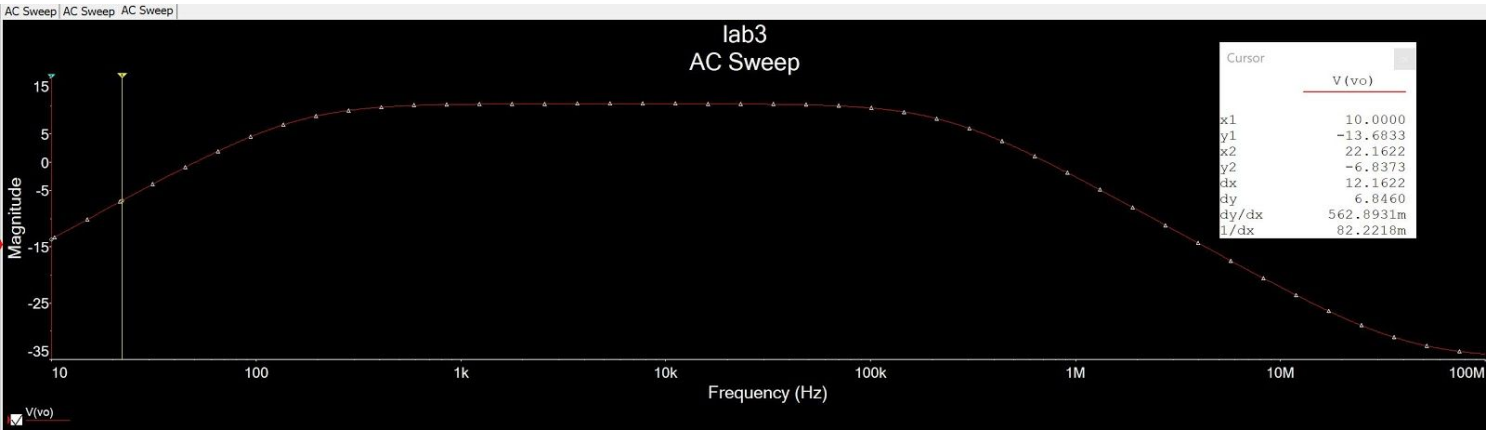


100Hz

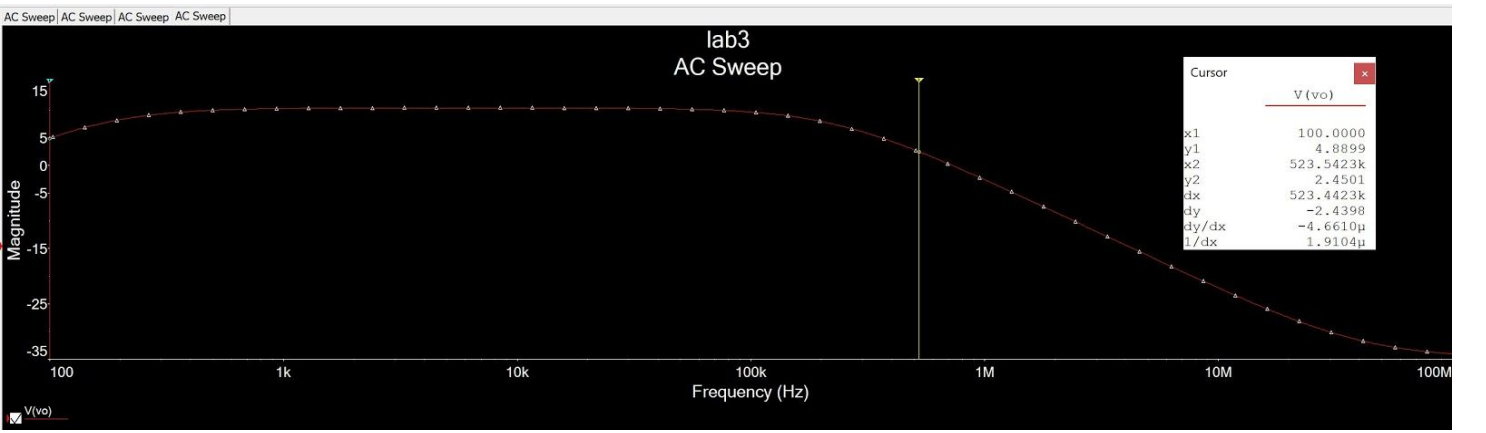

1KHz

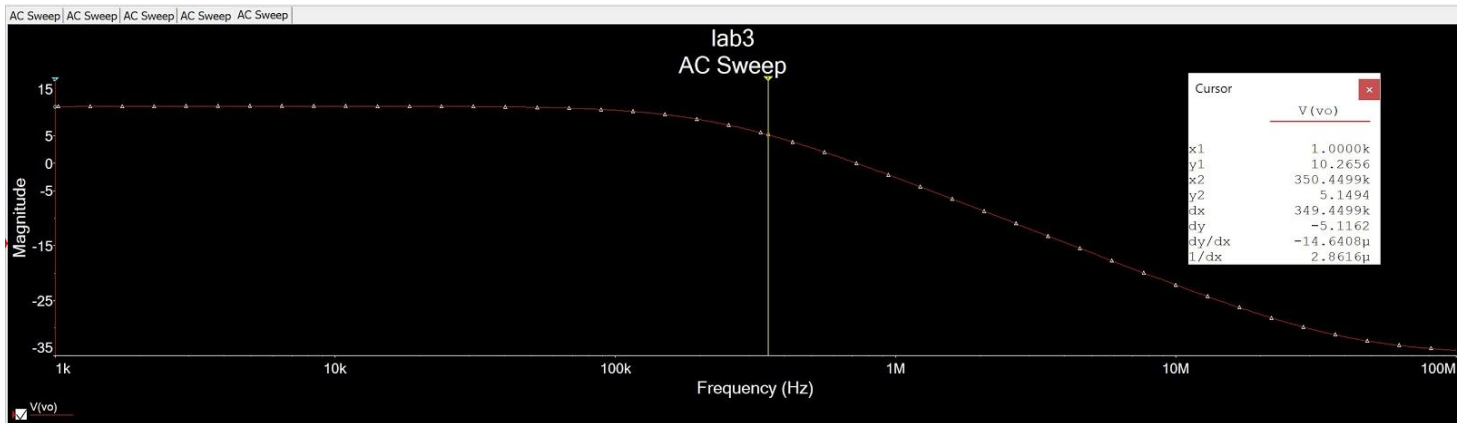


100KHz

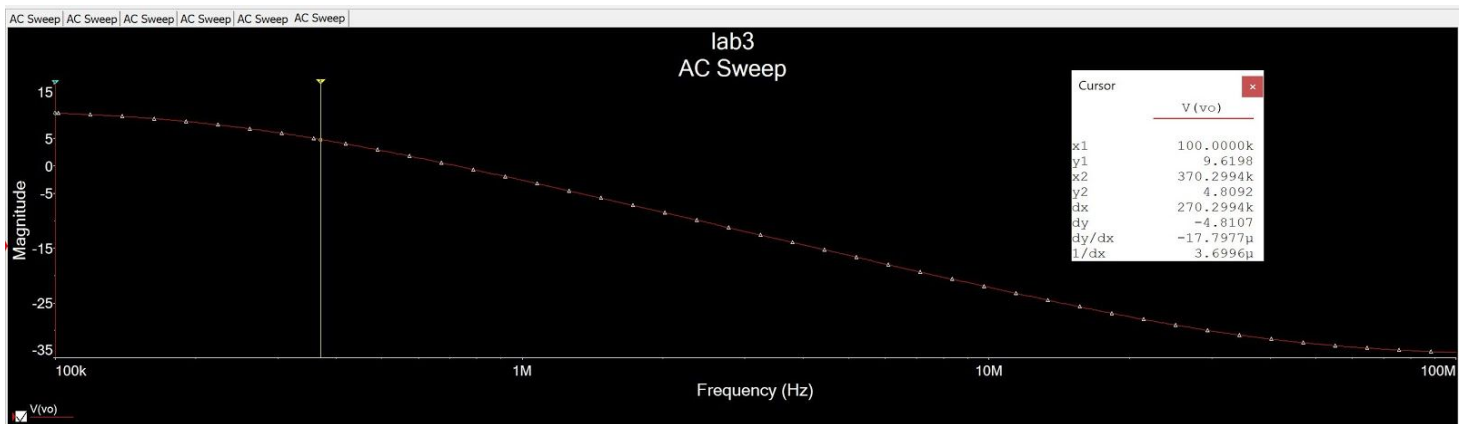


Level Shifting High Pass Filter:


10Hz

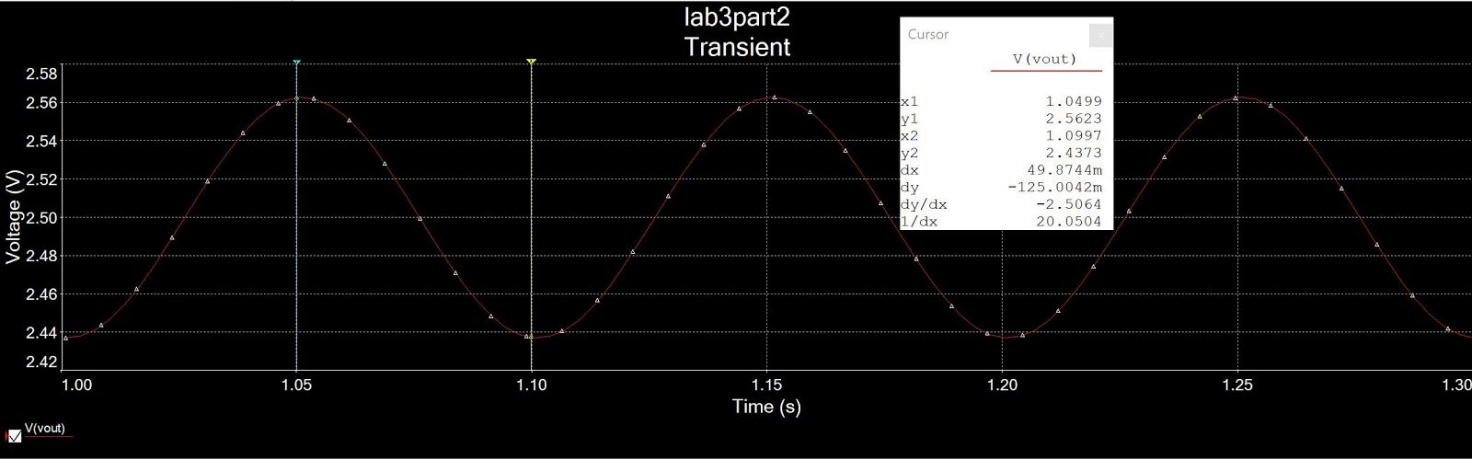


100Hz

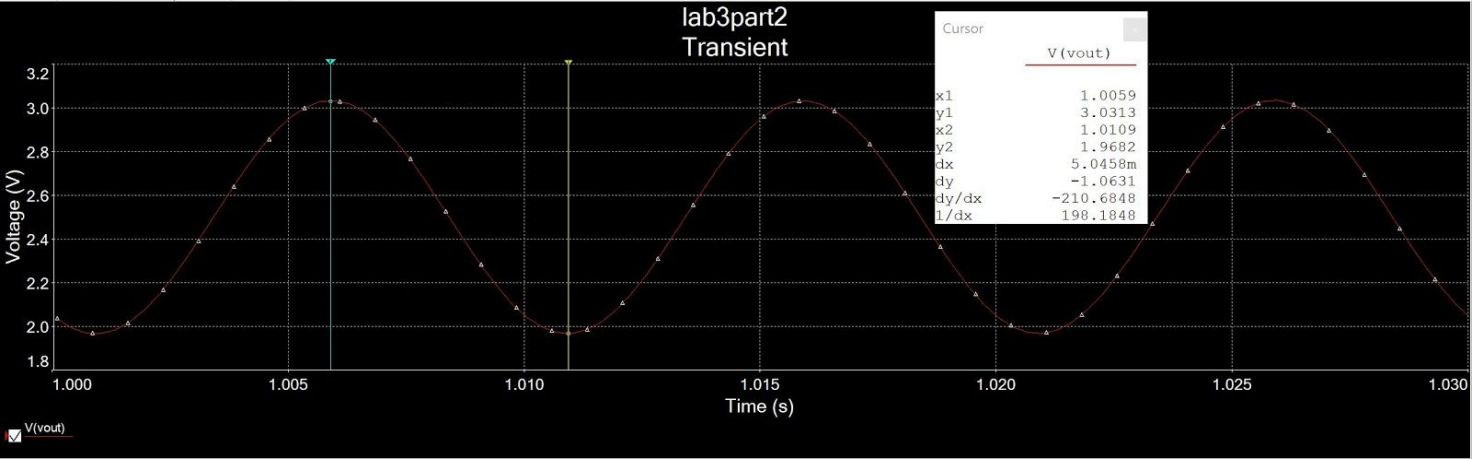

156Hz

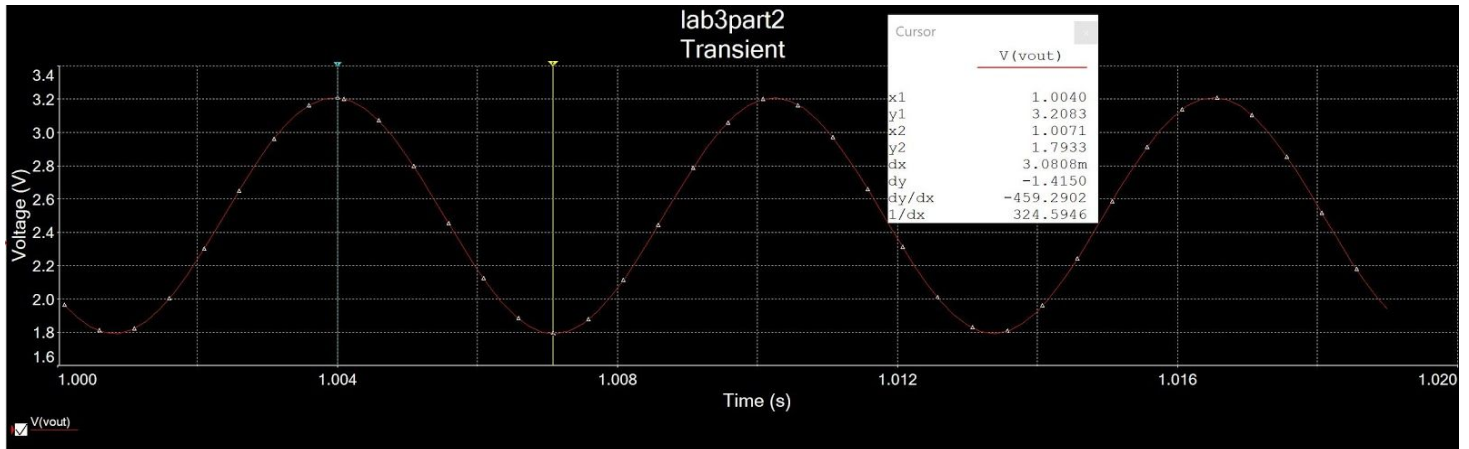

1KHz

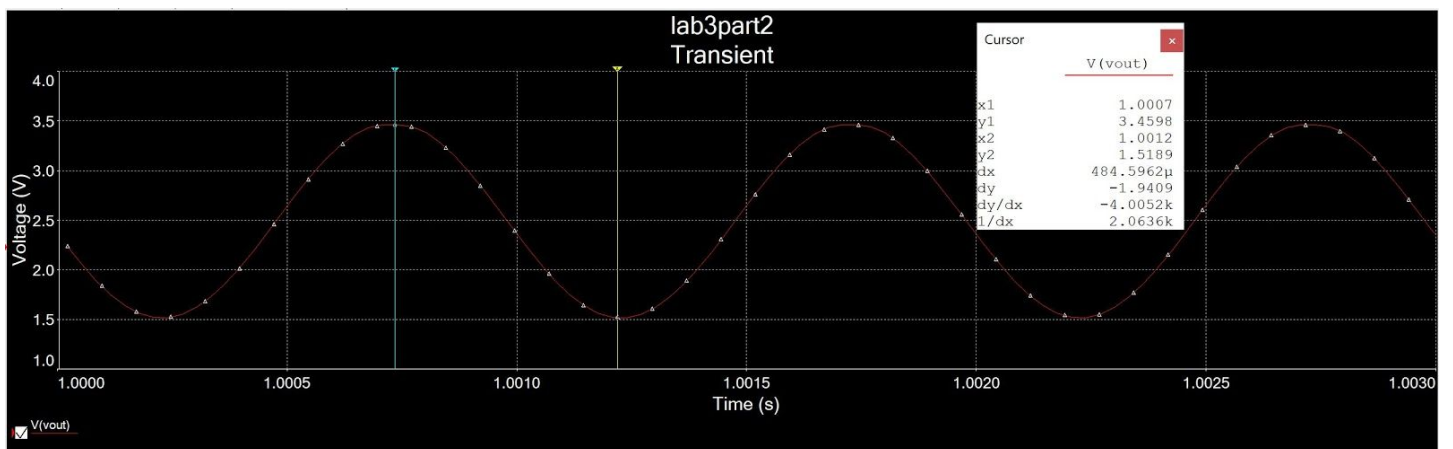

10KHz

